


University Of Texas At Austin

Schematic Name: Lab 6 Starter file


Name(s): Nikhil Garg and Nikhil Joglekar

Date: 10/5/12 Semester: Fall 2012
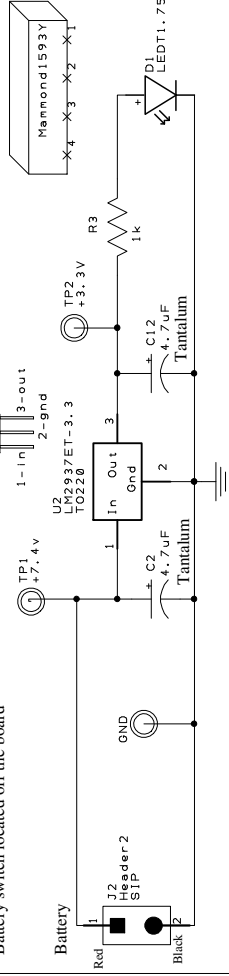
<http://www.hammondmfg.com/pdf/1593Y.pdf>



All Electronics DHS-40 cut in half

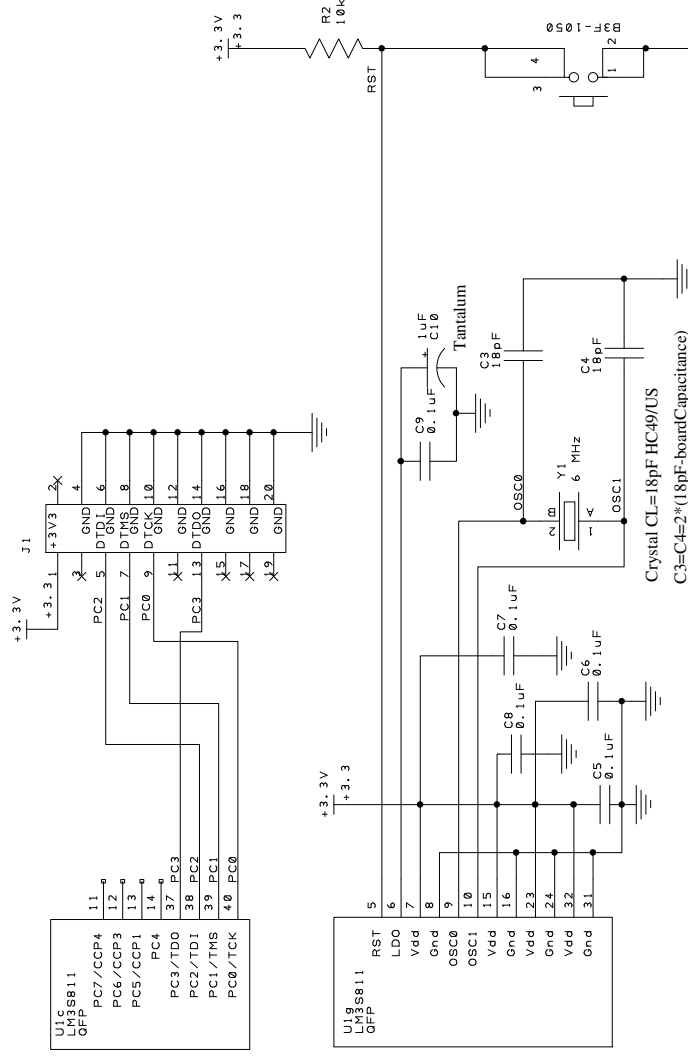

Unless otherwise noted, all capacitors are ceramic Z5U  
Unless otherwise noted, all resistors are carbon 5% 1/6 watt

<b>University Of Texas At Austin</b>	
<b>Schematic Name:</b>	Lab 6 starter file Power Clock JTAG
<b>Name(s):</b>	Put your name here or look silly
<b>Date:</b>	10/5/12 <b>Semester:</b> Fall 2012