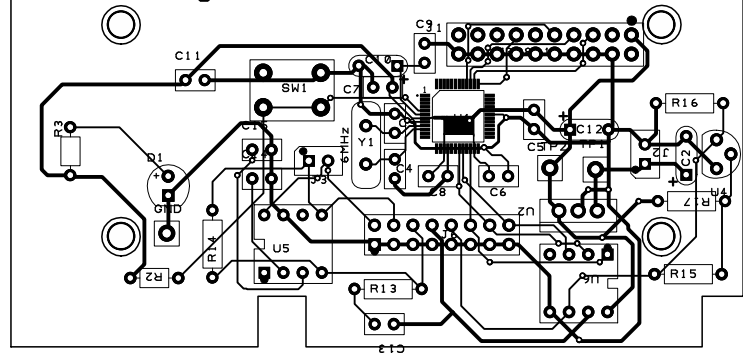


Box1



Nikhil Garg and Nikhil Joglekar
TA: Pohan & Victoria
10/14/2013 DAC and Speaker System



Battery

Your name
EE445L Lab 6
Oct 2012

University of Texas at Austin

Reset Logic Analyzer